

Interfacing the ADS786x to the MSP430F2013

Tom Hendrick

Data Acquisition Products

ABSTRACT

This application report presents methods of interfacing the ADS7866/67/68 12/10/8-bit SAR analog-to-digital converter to the MSP430F2013 universal serial interface (USI) in SPI mode. The flexible clocking scheme of the USI port, along with the internal 16-bit shift register, provides an easy hardware/software interface to this series of high-speed, micro-power SAR converters.

Contents

1	Introduction	1
2	Hardware	1
3	Software Interface	2
4	Power and Performance	4
5	Conclusion	4
6	References	4

List of Figures

1	Hardware Interface Block Diagram	2
2	Complete Conversion Cycle – Single Channel	4

List of Tables

1	Cable Requirements	2
---	--------------------------	---

1 Introduction

The ADS7866/67/68 are low-power, miniature, 12/10/8-bit A/D converters, each with a unipolar, single-ended input. These devices can operate from a single 1.6-V to 3.6-V supply with a 200-KSPS throughput for ADS7866. These devices can maintain at least a 100-KSPS throughput with a supply as low as 1.2 V, making them ideal candidates for low-power MSP430 applications requiring high-speed data acquisition.

MSP430 devices such as the new MSP430F2013, which contain a universal serial interface (USI), can be used in a simple and straightforward interface that requires no *glue logic* and little software overhead.

2 Hardware

The hardware used to produce the timing diagrams found throughout this application report includes the eZ430-F2013 Development Tool and the ADS7866/67/68 evaluation module (EVM).

2.1 ADS7866/67/68EVM

The ADS7866/67/68EVM is a member of the modular EVM series of serial ADCs available from Texas Instruments. The EVM provides a platform to demonstrate the functionality of the ADS7866, ADS7867, or ADS7868 ADC with various Texas Instruments DSPs and microcontrollers, while allowing easy access to all analog and digital signals for customized end-user applications. For more information on the EVM, see the user's guide [SLAU181](#).

2.2 eZ430-F2013 Development Tool

The eZ430-F2013 is a complete MSP430 development tool including all the hardware and software necessary to evaluate the MSP430F2013. The hardware is provided in a convenient USB stick form factor. The eZ430-F2013 uses the IAR Embedded Workbench™ Integrated Development Environment (IDE) to provide full emulation with the option of designing with a stand-alone system or detaching the removable target board to integrate into an existing design. To learn more about the tool, search the Texas Instruments home page for *eZ430*.

2.3 Hardware Interface

A simple three-wire interface is the minimum requirement to connect the eZ430-F2013 and the ADS7866/67/68 EVM. [Figure 1](#) shows the hardware connections. The chip select (\overline{CS}), serial data output (SDO), and serial clock (SCLK) pins from the ADC are connected to SDO, serial data in (SDI), and SCLK pins, respectively, of the USI port.

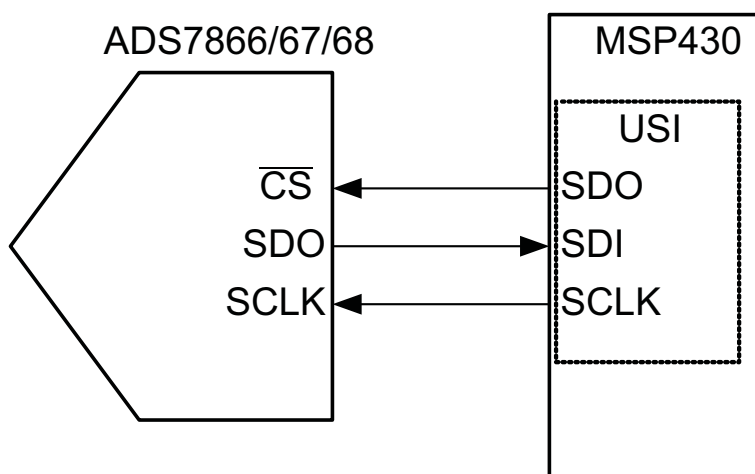


Figure 1. Hardware Interface Block Diagram

Table 1. Cable Requirements

ADS7866/67/68EVM	eZ430-F2013
J2.1 – Chip Select	P1.6 - SDO (GPIO is alternate choice)
J2.3 – CLOCK	P1.5 - SCLK
J2.13 – Data Out	P1.7 - SDI

3 Software Interface

The software was written and compiled using the Kickstart version of Embedded Workbench™ for the MSP430 from IAR. This software is the free version of the IDE and is available for download from the TI Web site, <http://www.ti.com>. The code used in these examples is available on request.

3.1 USI Settings

USI Control registers 0 and 1 (USICTL0 and USICTL1) set up the basic operation of the serial interface. The port is configured in SPI master mode by setting bits 3, 5, 6, and 7 in USICTL0. The USI Counter Interrupt is set in USICTL1 to provide an efficient means of SPI communication with minimal software overhead.

The serial clock polarity, source, and speed are controlled by settings in the USI Clock Control register (USICKCTL). For the purposes of this document, the polarity of the clock is set to one (dwells high) and the clock source was the SMCLK with a division factor of one.

Bit clocking and shift register configuration is controlled in the USI port by the bit settings in the USI Bit Count register (USICNT). By setting the USICNT to 0x11, 17 serial clocks are transmitted from the MSP430 to the ADS7866/67/68 on each conversion cycle. Setting the USI16B bit in the USICNT register causes the shift register to act as a 16-bit transmit/receive buffer. Transmitted data is MSB aligned and commences with the first SCLK cycle.

3.2 Starting a Conversion

Connecting the SDO output of the USI port to the \overline{CS} input on the ADS7866/67/68EVM starts a conversion cycle with timing fixed to the USI port transmitter. This ensures adequate setup time for the ADC to resume operation from its auto power-down state and provides three SCLK periods of sample time. The conversion results are presented on the serial data output pins of the ADC at the start of the sixth SCLK cycle.

The \overline{CS} pin also can be controlled by GPIO. In this case, care must be taken to ensure proper setup and hold times are met. Using GPIO to control the start of conversion allows the user to implement a 16 SCLK transfer by setting USICNT to 0x10. This would be useful in situations where additional slave SPI devices, such as a DAC, are used in the system.

The ADC begins to output the conversion results (MSB first) on the fifth SCLK cycle after the \overline{CS} pin toggles. Because the shift register holds the last 16 bits of received data, the entire conversion result is captured (LSB aligned) for further processing. [Figure 2](#) shows the entire process of this timing diagram.

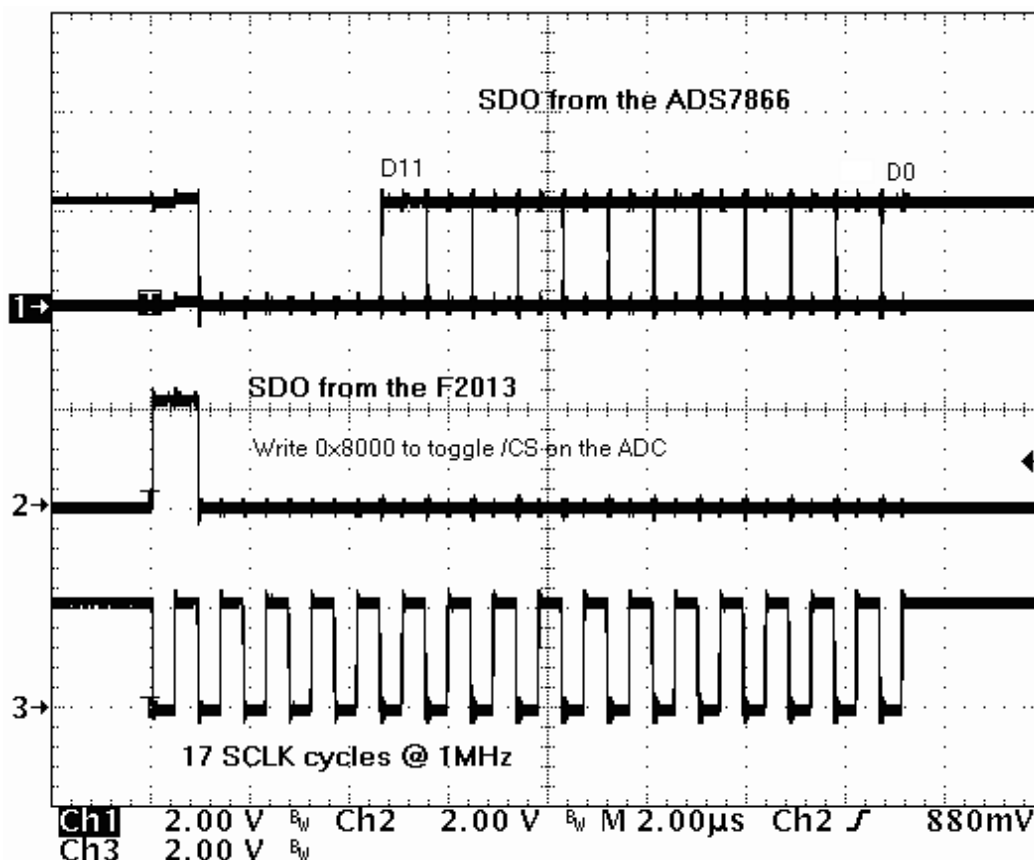


Figure 2. Complete Conversion Cycle – Single Channel

4 Power and Performance

The combining of low-power and high-performance ADS7866, ADS7867, and ADS7868 with the USI port of MSP430 processors is a relatively simple and straightforward task. System performance characteristics of 71-dB SNR, -83-dB THD, and ± 1.5 -LSB linearity are possible using as little power as 743 μ W.

For this application report, the MSP430F2013 target board from the eZ430-F2013 Development Kit and ADS7866 both were powered at 2.2 V. The ADC sample rate was approximately 24 KSPS. Total current drawn from the 2.2V supply was approximately 337.5 μ A, the ADS7866 drew 85.5 μ A.

5 Conclusion

The combining of low-power and high-performance ADS7866, ADS7867, and ADS7868 with the USI port of MSP430 processors is a relatively simple and straightforward task. In low-power or battery applications requiring high-performance data acquisition, the combination of the MSP430 and ultralow power ADCs from Texas Instruments provides a perfect combination of price and performance.

6 References

1. ADS7866/67/68 data sheet ([SLAS465](#))
2. MSP430Fx2xx User's Guide ([SLAU144](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2006, Texas Instruments Incorporated